

## METAL OXIDE SEMICONDUCTOR FIELD EFFECT TRANSISTORS (MOSFETS) AND COMMON ELECTRONIC CIRCUITS

1. What percentage of today's electronic circuits uses MOSFETs?
  - a. 75%
  - b. 80%
  - c. 90%
  - d. 100%
  
2. Heterojunction bipolar transistors (HBT's) are the
  - a. Fastest devices made
  - b. Only used in older equipment
  - c. Simplest devices made
  - d. Smallest devices made
  
3. How many MOSFETs can be put in the same physical area as a single BJT?
  - a. 25
  - b. 50
  - c. 100
  - d. 200
  
4. List three reasons why MOSFETs are favored over BJTs.
  
5. Because of their smaller size, MOSFET circuits have been able to reach frequencies as high as
  - a. 1 GHz
  - b. 1 MHz
  - c. 1 THz
  - d. 100 MHz
  
6. The lower power required by MOSFETs has led to an increase in
  - a. Battery size
  - b. Physical size
  - c. Portable devices
  - d. Stationary devices
  
7. The input impedance of a MOSFET gate is:
  - a. Relatively low (ohms)
  - b. Mid range (K ohms)
  - c. Relatively high (M ohms)
  - d. Can vary across all ranges



8. Since a MOSFET gate draws almost no current, the device
  - a. Moderately “loads” the driving circuit
  - b. Does not “load” the driving circuit
  - c. Heavily “loads” the driving circuit
  - d. Needs it’s own driving circuit
  
9. The input impedance to a MOSFET is seen as
  - a. A capacitor
  - b. An inductor
  - c. A large resistor
  - d. Unimportant
  
10. MOSFET circuits can be constructed without resistors.
  - a. True
  - b. False
  
11. What is the main disadvantage of a MOSFET??
  
  
12. The only area in which BJT’s outperform MOSFETs is in
  - a. Digital applications
  - b. High frequency applications (>10GHz)
  - c. Microprocessors
  - d. Wireless applications
  
13. The feature size of most current MOSFETs is as low as
  - a. 0.5 micron
  - b. 0.25 micron
  - c. 0.13 micron
  - d. 0.01 micron
  
14. Which type of MOSFET is the most widely used?
  - a. Depletion mode
  - b. Enhancement mode
  - c. N type
  - d. P type
  
15. In an N channel MOSFET, the source and drain are both N type material.
  - a. True
  - b. False



16. In an N channel MOSFET, a thin layer of \_\_\_\_\_ is placed between the substrate and the gate.
- Metal
  - N type silicon
  - P type silicon
  - SiO<sub>2</sub>
17. The gate of a MOSFET is made of a/an
- Highly conductive material
  - Insulating material
  - Semiconducting material
18. In order for an N channel E-MOSFET to conduct, the voltage applied to the gate must be
- Extremely high
  - Greater than the threshold voltage
  - Greater than zero
  - Negative
19. When a positive voltage is applied to the gate, electrons are attracted from the \_\_\_\_\_, which creates an induced channel under the gate.
- Drain
  - Gate
  - Source
  - Substrate
20. For a given  $V_{GS}$ , the drain current of a MOSFET will increase as the  $V_{DS}$  increases while in the \_\_\_\_\_ region.
21. Once the drain current no longer increases, the MOSFET is in the \_\_\_\_\_ region.
22. The point where  $V_{DS} = V_{GS} - V_T$  is called the \_\_\_\_\_ voltage.
- Beta
  - Cutoff
  - Ohmic
  - Pinch off
23. In order to calculate the drain current ( $I_D$ ), you need
- Beta,  $V_{GS}$  and  $V_T$
  - Beta,  $V_{GS}$  and  $V_{DS}$
  - $V_{GS}$ ,  $V_{DS}$  and  $V_T$
  - $V_T$ , Beta and  $V_P$



24. In linear circuits, a MOSFET will operate in the \_\_\_\_\_ region.
25. In digital circuits, a MOSFET will alternate between the
- Ohmic and cutoff region
  - Ohmic and saturation region
  - Saturation and cutoff region
26. What are linear circuits predominately used for?
27. A common linear circuit is an enhancement mode common source MOSFET. What two quantities are applied to the gate?
- DC bias voltage and input signal
  - DC bias voltage and resistive load
  - Input signal and resistive load
  - None of the above
28. In enhancement mode common source MOSFETs, the voltage gain produced is typically
- 1 to 5
  - 2 to 10
  - 10 to 25
  - Greater than 100
29. MOSFETs are usually designated by the letter
- M
  - Q
  - R
  - T
30. Drain resistors are commonly replaced by another MOSFET because the
- Circuit will respond faster
  - Resistor values are limited
  - Resistors are very unstable
  - Resistors takes up 100X more space
31. In order to use a MOSFET as a drain resistor, you must
- Apply the appropriate bias voltage
  - Connect the gate to the drain
  - Neither of the above
  - Both of the above



32. A MOSFET divider circuit has
- 2 MOSFETs in series with a drain resistor
  - 2 MOSFETs connected in parallel
  - 2 MOSFETs connected in series
  - 3 MOSFETs connected in parallel
33. When a MOSFET circuit is used as a current source, it
- Draws a fixed input current
  - Draws a variable input current
  - Provides a fixed output current to a load
  - Provides a variable output current to a load
34. A current sink is a circuit which
- Draws a constant current
  - Draws a constant voltage across it
  - Provides a constant output current
  - Provides a constant voltage across it
35. A current mirror is a circuit which
- Distributes equal current to bias more than one MOSFET
  - Is rarely used
  - Is very complex
  - Requires many resistors to distribute equal current
36. One of the most widely used amplifier configurations is the
- Averaging amplifier
  - Differential amplifier
  - Integrator
  - Summing amplifier
37. What is the output voltage to a differential amplifier with a gain of 10,  $V_1 = 5$  volts and  $V_2 = 7$  volts?
- 2 volts
  - 12 volts
  - 35 volts
  - 2 volts
38. What are the two main advantages of a cascade amplifier?
39. The Miller effect creates a capacitance at the amplifier input which
- Creates a high pass filter which increases the frequency response
  - Creates a low pass filter which limits the frequency response
  - Has little impact on the amplifier operation
  - Reduces the gain of the amplifier



40. The Miller effect can be eliminated by
  - a. Increasing the number of amplifiers
  - b. Putting another capacitor in parallel
  - c. Shorting out the capacitor
  - d. Using a cascade connection
  
41. A common application for the source follower amplifier is
  - a. For impedance matching
  - b. To increase drain current
  - c. To provide a high voltage gain
  - d. None of the above
  
42. How many MOSFETs does a push pull power amplifier use to create the output signal?
  - a. One
  - b. Two
  - c. Three
  - d. Four
  
43. The push-pull amplifier operates as a
  - a. Class A amplifier
  - b. Class AB amplifier
  - c. Class B amplifier
  - d. Class C amplifier
  
44. In a push pull power amplifier, crossover distortion is eliminated by
  - a. Applying a bias voltage that is approximately equal to the threshold voltage
  - b. Applying a bias voltage that is much larger than the threshold voltage
  - c. Applying the bias voltage to only one MOSFET
  - d. Eliminating the bias voltage
  
45. The open loop gain of a MOSFET operational amplifier is typically as high as
  - a. 1,000
  - b. 10,000
  - c. 100,000
  - d. 1 million
  
46. MOSFET op amps are typically powered by
  - a. A positive supply voltage
  - b. A negative supply voltage
  - c. Both a and b
  - d. Neither a nor b



47. The MOSFET switch is the main component in all
- Digital circuits
  - Linear and digital circuits
  - Linear circuits
  - Real time circuits
48. For an N channel MOSFET, when the gate voltage is zero, the MOSFET is \_\_\_\_ and the output is high.
- On
  - Off
  - Unable to determine
49. MOSFET switches are used to turn other devices on or off.
- True
  - False
50. Spike suppressor diodes are used to
- Protect the MOSFET
  - Protect the relays or other devices
  - Protect the user
  - Protect the wiring
51. The H bridge configuration can be used to energize two MOSFETS at one time in order to
- Control the direction of a DC Motor
  - Protect a DC motor from too much heat
  - Turn a DC motor off and on
  - None of the above
52. The CMOS circuit uses both N and P channel MOSFETS which are used as an
- Current mirror
  - Differential amplifier
  - Inverter
  - Power amplifier
53. The CMOS inverter is the basis for
- A few digital logic circuits
  - All linear circuits
  - Almost all amplifiers
  - Almost all digital logic circuits
54. If the input to a CMOS inverter is +5 volts, the output will be \_\_\_\_\_ volts.
- +2.5
  - +5
  - 0
  - 5



55. The BiCMOS is a combination of
- Bipolar transistors and CMOS logic circuits
  - N channel and P channel MOSFETS
  - Two or more logic circuits
  - Various inverter circuits
56. In a BiCMOS, the bipolar transistors are used as the
- Energizing circuit
  - Feedback circuit
  - Input circuit
  - Output circuit
57. The transmission gate is made with an N channel MOSFET in
- Parallel with a P channel MOSFET
  - Parallel with another N channel MOSFET
  - Series with a P channel MOSFET
  - Series with another N channel MOSFET
58. If the control input to a transmission gate is positive
- Both MOSFETs conduct
  - Neither MOSFET conduct
  - The N channel MOSFET conducts
  - The P channel MOSFET conducts
59. Name one common application for the transmission gate circuit.
60. In a sample/hold circuit, when the control input returns to zero, the capacitor
- Discharges back to zero
  - Holds the last voltage value
  - Is unaffected
  - Starts to charge up
61. Why are MOSFETs sensitive to static electricity?
62. List three methods to protect a MOSFET from static electricity.